

数字逻辑设计与微处理器系统 第五讲 Hardware Description Languages

马 上

通信抗干扰技术国家级重点实验室

mashang@uestc.edu.cn

Office: B3-510, Main Building

Tel (O) : 61830321

2021年4月

Contents




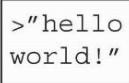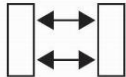
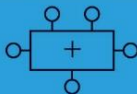

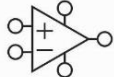
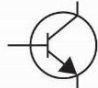

1. Introduction

- 1.1 Verilog Introduction
- 1.2 Verilog Basis
- 1.3 Structural Modeling

2. Application

- 2.1 Sequential Logic
- 2.2 More Combinational Logic
- 2.3 Finite State Machines
- 2.4 Parameterized Modules
- 2.5 Testbenches

3. Tools-ISE/Vivado

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

1.1 Verilog Introduction

- ★ **Hardware description language (HDL):**
 - ★ specifies logic function only
 - ★ Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
- ★ **Most commercial designs built using HDLs**
- ★ **Two leading HDLs:**
 - ★ **SystemVerilog/Verilog**
 - ★ developed in 1984 by Gateway Design Automation
 - ★ IEEE standard (1364) in 1995
 - ★ Extended in 2005 (IEEE STD 1800-2009)
 - ★ **VHDL 2008**
 - ★ Developed in 1981 by the Department of Defense
 - ★ IEEE standard (1076) in 1987
 - ★ Updated in 2008 (IEEE STD 1076-2008)

1.1 Verilog Introduction

- What & Why HDL?
- Verilog HDL
 - Modul Concept and structure
 - Identifier, Data Representation, Data Type
 - Mathematical symbol
- Abstraction Levels
 - Gates
 - Dataflow
 - Procedural

1.1 What & Why HDL?

- Hardware Description Language(HDL)
 - A software programming language used to model the intended operation of a piece of hardware
- Why HDL?
 - Text-based design rather than Schematic design
 - ASIC complexity increase
 - faster time-to-market
 - Simulation
 - Logic Synthesis
 - Words are better than pictures
 - PLD, CPLD and FPGA became inexpensive and commonplace

1.1 What is need for HDL ?

- Model, Represent, And Simulate Digital Hardware
 - Hardware Concurrency
 - Parallel Activity Flow
 - Semantics for Signal Value And Time
- Special Constructs And Semantics
 - Edge Transitions
 - Propagation Delays
 - Timing Checks





1.1 History of HDL

- First HDL
 - PALASM, 1980s--Logic equation
- Then more complex (minimization, if-then-else statement)
 - CUPL (Complier Universal for Programmable Logic)
 - ABEL (Advanced Boolean Equation Language)
- Verilog HDL
- VHDL represents another high level language for digital system design.
 - VHDL = VHSIC HDL
 - VHSIC = Very High Speed Integrated Circuit


1.1 HDLs

- Software: Assembler → high-level language, like C, C++, Java
- Hardware: block diagram & schematic → HDL
- Efficient → Large, complex, abstraction
- HDL Tool Suits
 - Text editor
 - Compiler
 - Synthesizer
 - Simulator
 - Template generator
 - Schematic viewer
 - Translator
 - Timing analyzer
 - Back annotator

1.1 Design flow

    


设计创意
+
仿真验证

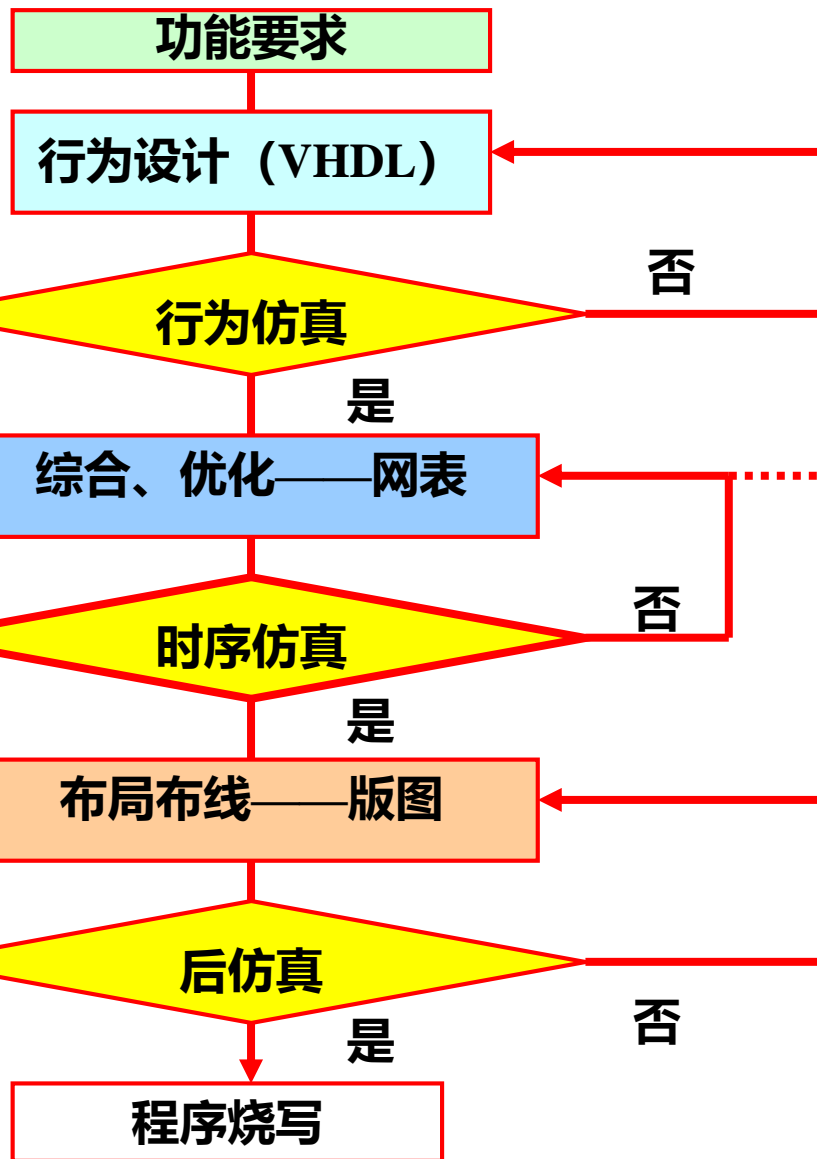

 1.1 Introduction to Verilog HDL

- Originally designed in 1983/1984 as a proprietary verification /simulation
- IEEE standard 1364 in 1995
- Similar to C language
- 4 value logic (0, 1, x, z)
- HDL which provides a wide range of levels of abstraction
 - Architectural, Algorithmic, RTL, Gate, Switch
- Mixed level modeling and simulation
- Description of digital systems only
- Interactive usage
- Hierarchical specification



1.1 History

- 1981
 - Gateway Design Automation was founded
 - Phil Mooby make GHDL(GenRad's HDL) and HILO simulator
- 1983
 - Gateway released the Verilog HDL and simulator
- 1985
 - The language and simulator were enhanced and renamed to “Verilog-XL”
- 1988 synopsys make Verilog synthesis tool
- 1989
 - Cadence bought Gateway
- 1995
 - The Verilog HDL was adopted as IEEE standard 1364
 - i.e. Verilog-1995
- 1997, Verilog-2001

1.1 Verilog Spans a Wide Range of Modeling Levels


Increasing
level of
abstraction

- Architectural
- Algorithmic
- RTL
- Gate
- Switch

```
always #($dis_poisson(seed,32))
begin
  if $q_full(qid)
    $q_remove (qid, job, job_id, status);
  else
    → fill_queue;
end
```

```
always @(fetch_done)
begin
  casez (IR[7:6])
    2'b00 : LDA (acc, IR[5:0]);
    2'b01 : STR (acc,IR[5:0]);
    2'b10 : JMP (IR[5:0]);
    2'b11 : ; // NOP
  endcase
end
```

```
assign rt1 = (i1&buserr) | zero;
assign sub = rt1 ^| op;
assign out1 = i1 & i2 | op;
```

 

*behavioral
(non-structural)*

*gate/switch
(structural)*

1.1 HDL to Gates

★ Simulation

- ★ Inputs applied to circuit
- ★ Outputs checked for correctness
- ★ Millions of dollars saved by debugging in simulation instead of hardware

★ Synthesis

- ★ Transforms HDL code into a netlist describing the hardware (i.e., a list of gates and the wires connecting them)

IMPORTANT:

When using an HDL, think of the hardware the HDL should produce

1.2 Verilog Syntax

- ★ Case sensitive

- ★ Example: **reset** and **Reset** are not the same signal.

- ★ Formed from {[A-Z], [a-z], [0-9], _, \$}, but **can't begin** with \$ or [0-9]

- ★ myidentifier ☺

- ★ m_y_identifier ☺

- ★ 3my_identifier ☹️ ❌

- ★ \$my_identifier ☹️ ❌

- ★ _myidentifier\$ ☺

- ★ Whitespace ignored





1.2 Verilog Syntax

★ Comments:

```
// single line comment  
/* multiline  
    comment */
```


★ Verilog Value Set

    - ★ 0 represents low logic level or false condition
- ★ 1 represents high logic level or true condition
- ★ x represents unknown logic level
- ★ z represents high impedance logic level




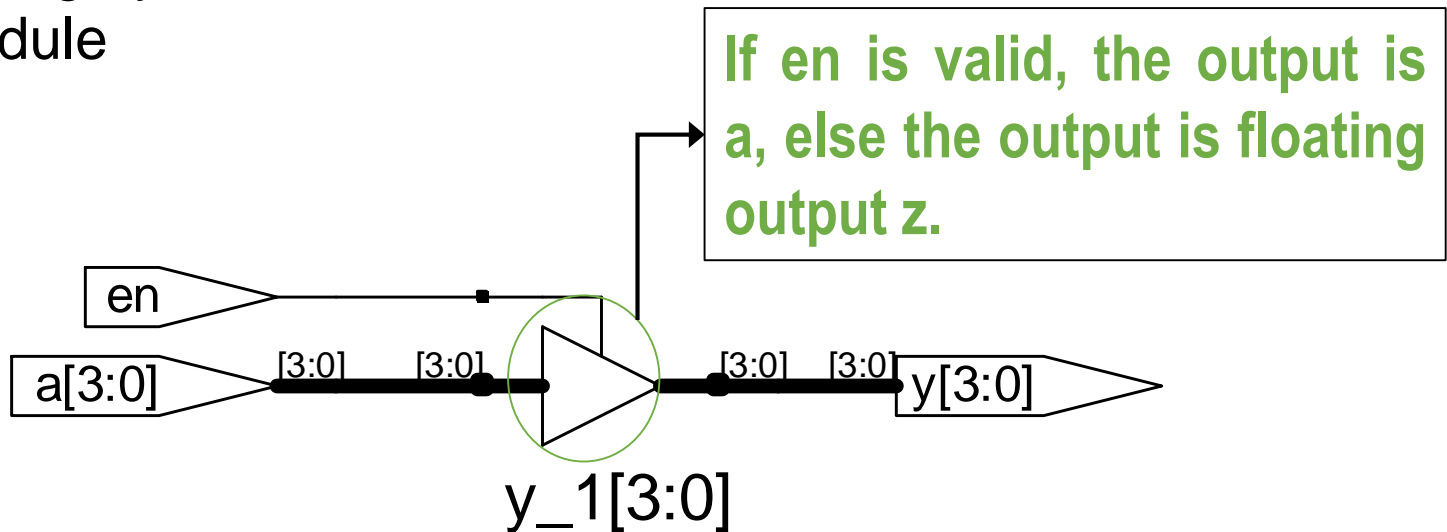1.2 Z: Floating Output

```
module tristate(input  [3:0] a, input en,  
                output [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```



1.2 Numbers in Verilog

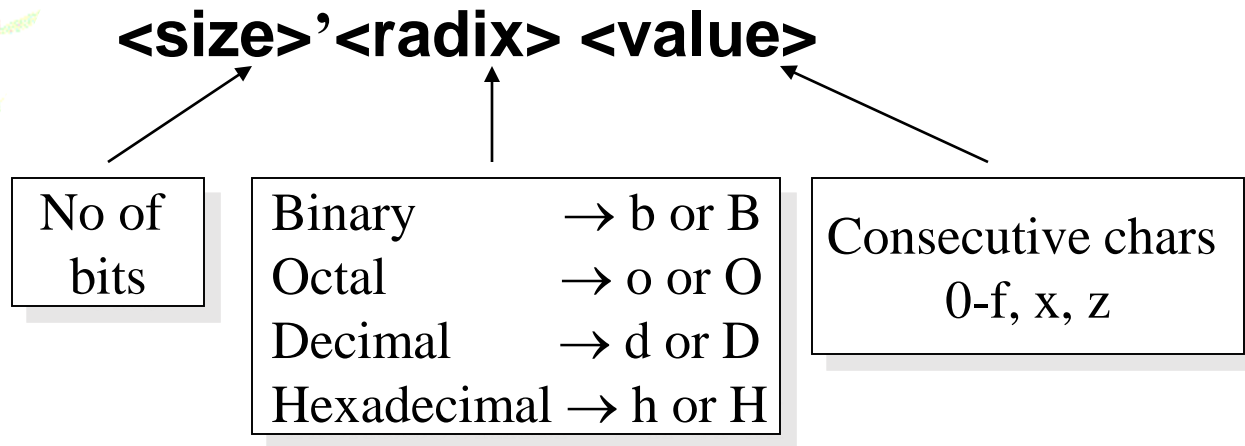

- ★ **8'h ax = 1010xxxx**

- ★ **12'o 3zx7 = 011zzzxxx111**

- ★ You can insert “_” **for readability**

- ★ **12'b 000_111_010_100**

- ★ **12'b 000111010100**

- ★ **12'o 07_24**

1.2 Numbers in Verilog

★ Bit extension

- ★ MS bit = 0, x or z \Rightarrow extend this

- ★ $4'b\ x1 = 4'b\ xx_x1$

- ★ MS bit = 1 \Rightarrow zero extension

- ★ $4'b\ 1x = 4'b\ 00_1x$

★ If *size* is omitted it

- ★ is inferred from the *value* or
- ★ takes the simulation specific number of bits or
- ★ takes the machine specific number of bits

★ If *radix* is omitted too .. decimal is assumed

- ★ $15 = \langle \text{size} \rangle'd\ 15$

1.2 Data Types

★ Nets

- ★ Connects between hardware elements
- ★ Must be continuously driven by
 - ★ Continuous assignment (assign)
 - ★ Module or gate instantiation (output ports)
- ★ Default initial value for a *wire* is “Z” (and for a *triereg* is “x”)

★ Registers

- ★ Represent data storage elements
- ★ Retain value until another value is placed on to them
- ★ Similar to “variables” in other high level language
- ★ Different to edge-triggered flip-flop in real circuits
- ★ Do not need clock
- ★ Default initial value for a *reg* is “X”


1.2 Nets

- Can be thought as **hardware wires** driven by logic
- Equal **z** when **unconnected**
- Various types of nets
 - **wire, tri** : standard
 - **wor, trior** : wired OR
 - **wand, triand** : wired AND
 - **triereg** : capacitive
 - **tri1** : pull up
 - **tri0** : pull down
 - **supply1** : power
 - **supply0** : ground


综合编译器
不支持
的net类型

 1.2 Nets

In following examples: **Y** is evaluated, *automatically*, every time **A** or **B** changes



 
```
wire Y; // declaration
assign Y = A & B;
```



```
wand Y; // declaration
assign Y = A;
assign Y = B;
```

		A	
Y		0	1
B	0	0	0
	1	0	1

 

```
wor Y; // declaration
assign Y = A;
assign Y = B;
```

		A	
Y		0	1
B	0	0	1
	1	1	1

```
tri Y; // declaration
assign Y = (dr) ? A : z;
```

1.2 Registers

- ★ **Variables** that store values
- ★ Do **not represent real hardware** but ..
- ★ .. real hardware can be implemented with registers
- ★ Only one type: **reg**

```
reg A, C; // declaration
```

```
// assignments are always done inside a procedure
```

```
A = 1;
```

```
C = A; // C gets the logical value 1
```

```
A = 0; // C is still 1
```

```
C = 0; // C is now 0
```

- ★ **Register values are updated explicitly!!**

1.2 Vectors

- ★ **Represent buses**

```
wire [3:0] busA;  
reg [1:4] busB;  
reg [1:0] busC;
```

- ★ **Left number is MS bit**

- ★ **Slice management**

```
busC[1] = busA[2];  
busC[0] = busA[1];
```

- ★ **Vector assignment (*by position!!*)**

```
busB[1] = busA[3];  
busB[2] = busA[2];  
busB[3] = busA[1];  
busB[4] = busA[0];
```

1.2 Register Types

★ Integer

- ★ **integer a,b; // declaration**
- ★ **32-bit signed (2's complement)**

★ real

- ★ **real c, d; //declaration**
- ★ **64-bit real number**
- ★ **Defaults to an initial value of 0.0**

★ Time

- ★ **64-bit unsigned, behaves like a 64-bit reg**
- ★ **\$display("At %t, value=%d", \$time, val_now)**

1.2 Integer & Real Data Types

- ★ **Declaration**

```
integer i, k;  
real r;
```

- ★ **Use as registers (inside procedures)**

```
i = 1; //assignments occur inside procedure  
r = 2.9;  
k = r; // k is rounded to 3
```

- ★ **Integers are not initialized!!**

- ★ **Reals are initialized to *0.0***

1.2 Time Data Type

- ★ **Special data type for simulation time measuring**

- ★ **Declaration**

```
time my_time;
```

- ★ **Use inside procedure**

```
my_time = $time; // get current sim time
```

- ★ **Simulation runs at simulation time, not real time**

1.2 Operators

Arithmetic Operators	$+, -, *, /, \%$
Relational Operators	$<, <=, >, >=$
Logical Equality Operators	$==, !=$
Case Equality Operators	$===, !==$
Logical Operators	$!, \&\&, $
Bit-Wise Operators	$\sim, \&, , \wedge(\text{xor}), \sim\wedge(\text{xnor})$
Unary Reduction Operators	$\&, \sim\&, , \sim , \wedge, \sim\wedge$
Shift Operators	$>>, <<$
Conditional Operators	$? :$
Concatenation Operator	$\{\}$
Replication Operator	$\{\{\}\}$

1.2 Bitwise Operators

★ &

→ **bitwise AND**

★ |

→ **bitwise OR**

★ ~

→ **bitwise NOT**

★ ^

→ **bitwise XOR**

★ ~ ^


^ ~

→ **bitwise XNOR**


★ **Operation on bit by bit basis**

1.2 Bitwise Operators


★ $a = 4'b1010;$
 $b = 4'b1100;$

 


$c = \sim a;$

 

$c = a \& b;$

 


$c = a \wedge b;$

 

zero
extended

★ $a = 4'b1010;$
 $b = 2'b11;$

 

1.2 Bitwise Operators

```
module gates(input [3:0] a, b,  
             output [3:0] y1, y2, y3, y4, y5);
```

```
/* Five different two-input logic  
gates acting on 4 bit busses */
```

```
assign y1 = a & b; // AND
```


```
assign y2 = a | b; // OR
```

```
assign y3 = a ^ b; // XOR
```

```
assign y4 = ~(a & b); // NAND
```

```
assign y5 = ~(a | b); // NOR
```

```
endmodule
```

 


1.2 Bit Manipulations

```
module mux2_8(input [7:0] d0, d1, input s,  
              output [7:0] y);
```

```
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
```

```
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
```

```
endmodule
```

 

1.2 Reduction Operators

★ &

→ AND

★ |

→ OR

★ ^

→ XOR

★ ~&

→ NAND

★ ~|

→ NOR

★ ~^ ^~

→ XNOR

★ **One multi-bit operand → One single-bit result**


```
a = 4'b1001;
```

```
..
```

```
c = |a; // c = 1|0|0|1 = 1
```

 
1.2 Reduction Operators

```
module and8(input [7:0] a, output y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    // a[3] & a[2] & a[1] & a[0];  
endmodule
```



1.2 Logical Operators

★ **& &** → logical AND

★ **| |** → logical OR

★ **!** → logical NOT

★ Operands **evaluated to ONE bit** value: 0, 1 or x

★ Result is **ONE bit** value: 0, 1 or x

★ All value should be **changed to true or false** before operate


★ $4'b0100 \ \&\& \ 4'b0101 \Rightarrow \text{true} \ \&\& \ \text{true} = \text{true}(1)$

★ $4'b0100 \ \& \ 4'b0101 = 4'b0100$

A = 6;

B = 0;

C = x;

 

A && B → 1 && 0 → 0

A || !B → 1 || 1 → 1

C || B → x || 0 → x



but C&&B=0

1.2 Shift Operators

★ `>>` → shift right

★ `<<` → shift left

★ Result is **same size** as first operand, always **zero filled**

Example:

```
a = 4'b1010;
```

```
...
```

```
d = a >> 2;    // d = 0010
```

```
c = a << 1;    // c = 0100
```

1.2 Concatenation Operator

★ **{op1, op2, ..}** → concatenates op1, op2, .. to **single number**

★ **Operands must be sized !!**

```
reg a;  
reg [2:0] b, c;  
..  
a = 1'b 1;  
b = 3'b 010;  
c = 3'b 101;  
catx = {a, b, c};           // catx = 1_010_101  
caty = {b, 2'b11, a};       // caty = 010_11_1  
catz = {b, 1};              // WRONG !!
```

★ **Replication ..**

```
catr = {4{a}, b, 2{c}};     // catr = 1111_010_101101
```

1.2 Relational Operators

★ $>$ → **greater than**

★ $<$ → **less than**

★ $>=$ → **greater or equal than**

★ $<=$ → **less or equal than**

★ **Result is one bit** value: *0*, *1* or *x*

$1 > 0$ → *1*

$'b1x1 <= 0$ → *x*

$10 < z$ → *x*

1.2 Equality Operators

- ★ `==` → **logical equality**
- ★ `!=` → **logical inequality**
- ★ `===` → **case equality**
- ★ `!==` → **case inequality**


★ **example**

- ★ `4'b 1z0x == 4'b 1z0x → X`
- ★ `4'b 1z0x != 4'b 1z0x → X`
- ★ `4'b 1z0x === 4'b 1z0x → 1`
- ★ `4'b 1z0x !== 4'b 1z0x → 0`

1.2 Conditional Operator


- ★ `cond_expr ? true_expr : false_expr`

- ★ Like a 2-to-1 mux ..

 

 1.2 Conditional Operator

```
module mux2(input [3:0] d0, d1, input s,  
            output [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```



? : is also called a *ternary operator* because it operates on 3 inputs: **s**, **d1**, and **d0**.

1.2 Arithmetic Operators

- ★ + → Arithmetic addition
- ★ - → Arithmetic subtraction
- ★ * → Arithmetic multiplication
- ★ / → Arithmetic division
- ★ % → Modular arithmetic
- ★ If any operand is x the result is x
- ★ Negative registers:
 - ★ regs can be **assigned negative but are treated as unsigned**

```
reg [15:0] regA;  
..  
regA = -4'd12;      // stored as  $2^{16}-12 = 65524$   
regA/3              // evaluates to 21841
```

1.2 Arithmetic Operators

★ Negative integers:

- ★ can be assigned negative values
- ★ different treatment **depending on base specification or not**

```
reg [15:0] regA;
```

```
integer intA;
```

```
..
```

```
intA = -12/3;    // evaluates to -4 (no base spec)
```


1.2 Internal Variables

```
module fulladder(input a, b, cin,  
                 output s, cout);  
    wire p, g; // internal nodes
```

```
    assign p = a ^ b;  
    assign g = a & b;
```

```
    assign s = p ^ cin;  
    assign cout = g | (p & cin);
```

```
endmodule
```

 

1.2 Precedence

Order of Operators


Highest



Lowest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

1.3 Verilog Modules

 

★ Two types of Modules:

- ★ Behavioral: describe what a module does
- ★ Structural: describe how it is built from simpler modules

1.3 Modules Declaration

```
module full_add (A, B, CI, S, CO) ;
```

```
input A, B, CI ;
```

```
output S, CO ;
```

```
wire N1, N2, N3;
```

```
half_add HA1 (A, B, N1, N2),  
          HA2 (N1, CI, S, N3);
```

```
or P1 (CO, N3, N2);
```

```
endmodule
```

```
module half_add (X, Y, S, C);
```

```
input X, Y ;
```

```
output S, C ;
```

```
xor (S, X, Y) ;
```

```
and (C, X, Y) ;
```

```
endmodule
```

1.3 Behavioral Verilog

★ Verilog:


```
module example(input a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

- ★ **module/endmodule:** required to begin/end module
- ★ **example:** name of the module
- ★ **Operators:**
 - ~: NOT
 - &: AND
 - |: OR

1.3 HDL Simulation

★ Verilog:

```
module example(input a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

 


1.3 HDL Synthesis


★ Verilog:

```
module example(input a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```


★ Synthesis:

 

1.3 Structural Modeling - Hierarchy

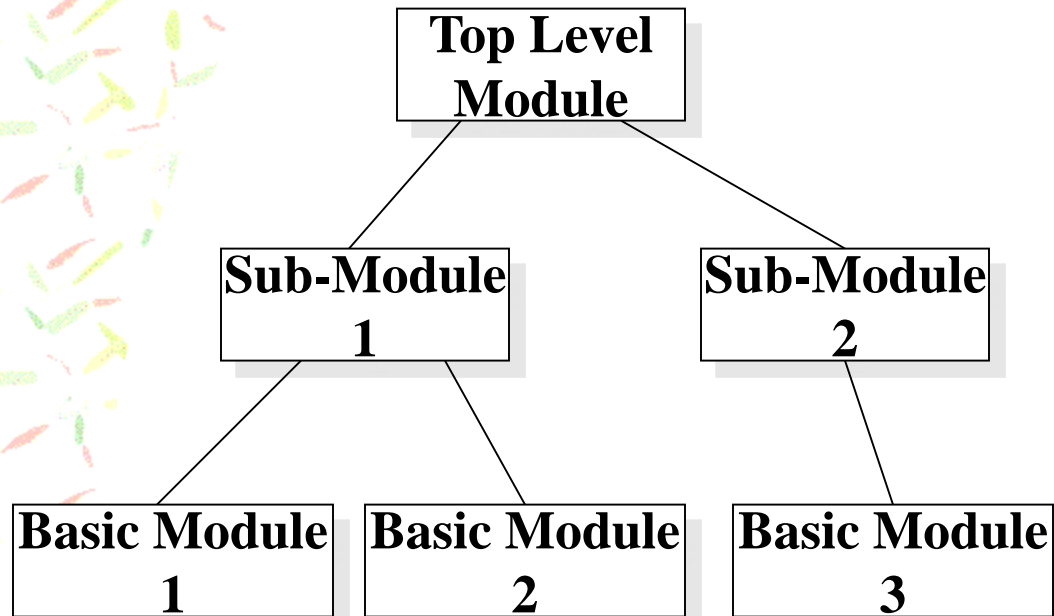

E.g.

 

⑩ Concurrency

⑩ Structure

⑩ Procedural Statements

⑩ Time


1.3 Structural Modeling - Hierarchy

```
module and3(input a, b, c, output y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input a, output y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input a, b, c output y);  
    wire n1;           // internal signal  
    and3 andgate(a, b, c, n1); // instance of and3  
    inv inverter(n1, y);  // instance of inv  
endmodule
```

2 Verilog Application

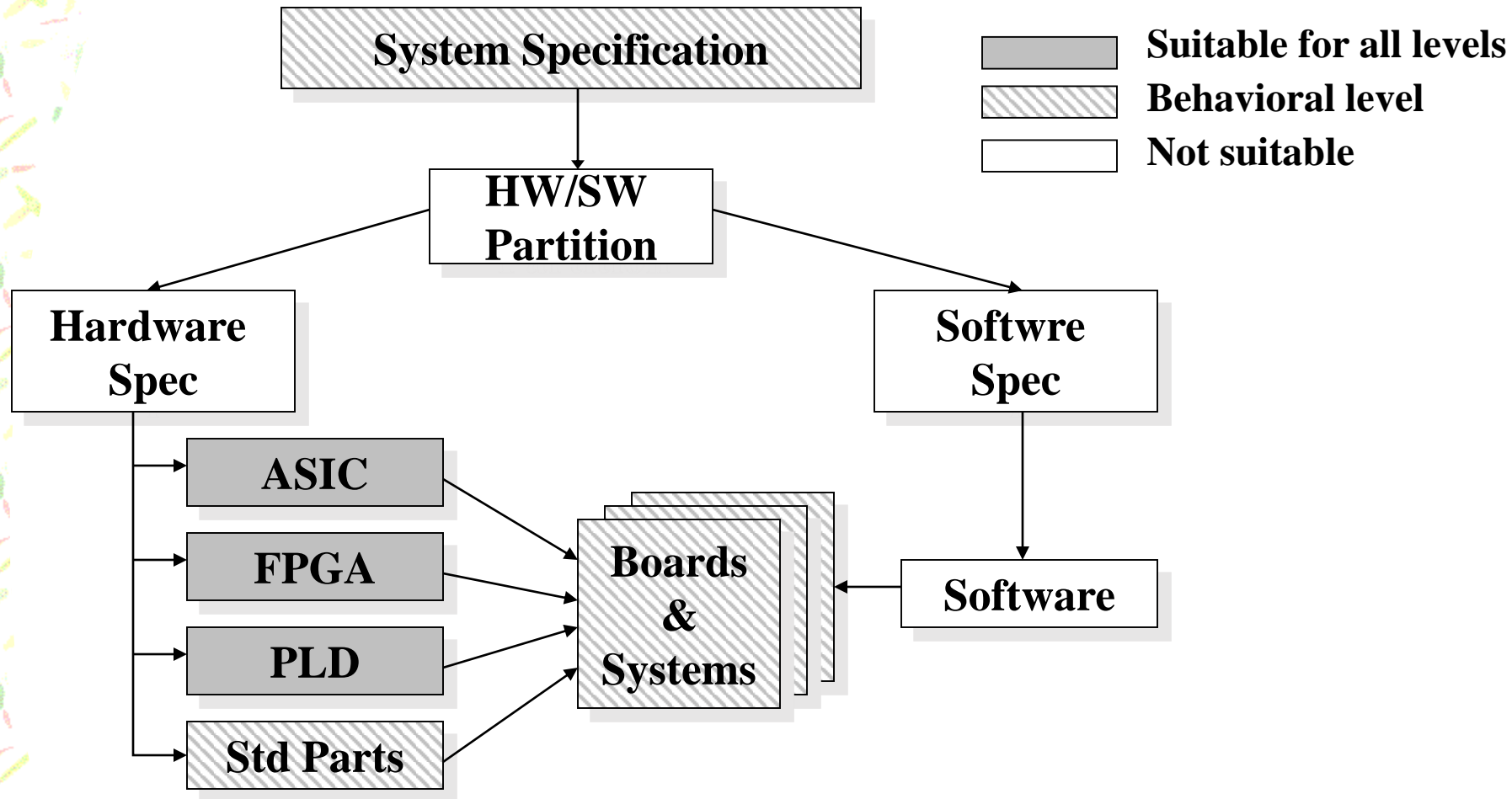

2.1 Sequential Logic

- ★ SystemVerilog uses **idioms** to describe latches, flip-flops and FSMs
- ★ Other coding styles may simulate correctly but produce incorrect hardware

2.1 Always Statement

General Structure:

```
always @ (sensitivity list)  
statement;
```

**Whenever the event in *sensitivity list* occurs,
statement is executed**


2.1 D Flip-Flop

```
module flop(input      clk,  
            input  [3:0] d,  
            output reg [3:0] q);
```

```
    always @(posedge clk)
```

```
        q <= d;           // pronounced “q gets d”
```

```
endmodule
```

 


2.1 Resettable D Flip-Flop

```
module flopr(input    clk,  
            input    reset,  
            input  [3:0] d,  
            output reg [3:0] q);
```

```
// synchronous reset
```

```
always@(posedge clk)  
    if (reset) q <= 4'b0;  
    else      q <= d;
```

```
endmodule
```

 

2.1 D Flip-Flop with Enable

```
module flopren(input      clk,  
               input      reset,  
               input      en,  
               input  [3:0] d,  
               output reg [3:0] q);
```


// asynchronous reset and enable

```
always @(posedge clk, posedge reset)
```

```
    if (reset) q <= 4'b0;
```

```
    else if (en)  q <= d;
```

```
endmodule
```

 


2.1 Latch

```
module latch(input      clk,  
             input  [3:0] d,  
             output reg [3:0] q);
```

```
    always@(clk,d)  
        if (clk) q <= d;
```

```
endmodule
```

 

2.1 Other Behavioral Statements

- ★ **Statements that must be inside always statements:**
 - ★ **if / else**
 - ★ **case, casez**

2.2 Combinational Logic using always

// combinational logic using an always statement

```
module gates(input  [3:0] a, b,  
              output reg [3:0] y1, y2, y3, y4, y5);  
    always@(*)    // need begin/end because there is  
    begin        // more than one statement in always  
        y1 = a & b;    // AND  
        y2 = a | b;    // OR  
        y3 = a ^ b;    // XOR  
        y4 = ~(a & b); // NAND  
        y5 = ~(a | b); // NOR  
    end  
endmodule
```

This hardware could be described with assign statements using fewer lines of code, so it's better to use assign statements in this case.

2.2 Combinational Logic using case

```
module sevenseg(input  [3:0] data,
                 output reg [6:0] segments);

    always@(*)
        case (data)
            0: segments = 7'b111_1110;           // abc_defg
            1: segments = 7'b011_0000;
            2: segments = 7'b110_1101;
            3: segments = 7'b111_1001;
            4: segments = 7'b011_0011;
            5: segments = 7'b101_1011;
            6: segments = 7'b101_1111;
            7: segments = 7'b111_0000;
            8: segments = 7'b111_1111;
            9: segments = 7'b111_0011;
            default: segments = 7'b000_0000; // required
        endcase
    endmodule
```

2.2 Combinational Logic using case

- ★ **case statement implies combinational logic only if all possible input combinations described**
- ★ **Remember to use default statement**

2.2 Combinational Logic using casez

```
module priority_casez(input  [3:0] a,  
                     output reg [3:0] y);
```

```
  always@(*)
```

```
    casez(a)
```

```
      4'b1???: y = 4'b1000; // ? = don't care
```

```
      4'b01??: y = 4'b0100;
```


```
      4'b001?: y = 4'b0010;
```

```
      4'b00001: y = 4'b00001;
```

```
      default: y = 4'b00000;
```

```
    endcase
```

```
endmodule
```

 

2.2 Blocking vs. Nonblocking Assignment

 **<= is nonblocking assignment**

 **Occurs simultaneously with others**


 **= is blocking assignment**

 **Occurs in order it appears in file**

 2.2 Blocking vs. Nonblocking Assignment


```
// Good synchronizer using
// nonblocking assignments
module syncgood(input clk,
                input  d,
                output reg q);

wire n1;
always @(posedge clk)
begin
    n1 <= d; // nonblocking
    q  <= n1; // nonblocking
end
endmodule
```



```
// Bad synchronizer using
// blocking assignments
module syncbad(input clk,
               input  d,
               output reg q);

 wire n1;
always @(posedge clk)
begin
    n1 = d; // blocking
    q  = n1; // blocking
end
endmodule
```



2.2 Rules for Assignment

- ★ **Synchronous sequential logic:** use `always @(posedge clk)` and nonblocking assignments (`<=`)

```
always @ (posedge clk)
q <= d; // nonblocking
```

- ★ **Simple combinational logic:** use continuous assignments (`assign...`)


```
assign y = a & b;
```

- ★ **More complicated combinational logic:** use `always@(*)` and blocking assignments (`=`)
- ★ **Assign a signal in only one always statement or continuous assignment statement.**

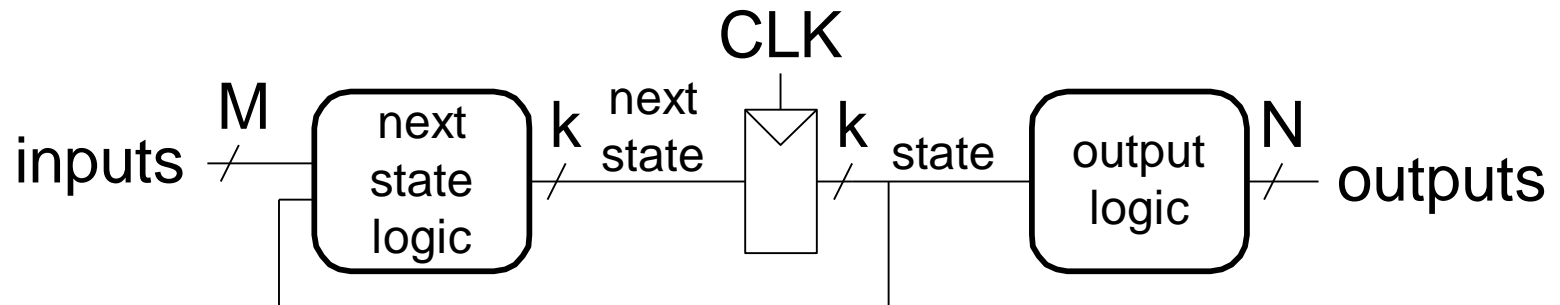
2.3 Finite State Machines(FSM)

★ Three blocks:

- ★ next state logic
- ★ state register
- ★ output logic



2.3 FSM example: Divide by 3

 

The double circle indicates the reset state

2.3 FSM in Verilog

```
module divideby3FSM (input clk,  
                    input reset,  
                    output q);
```

```
    reg [1:0] state, nextstate;
```

```
    parameter S0 = 2'b00;
```

```
    parameter S1 = 2'b01;
```

```
    parameter S2 = 2'b10;
```

```
    // state register
```

```
    always@ (posedge clk, posedge reset)
```

```
        if (reset) state <= S0;
```

```
        else      state <= nextstate;
```

```
    // next state logic
```

```
    always@(*)
```

```
        case (state)
```

```
            S0:  nextstate = S1;
```

```
            S1:  nextstate = S2;
```

```
            S2:  nextstate = S0;
```



```
            default: nextstate = S0;
```

```
        endcase
```

```
    // output logic
```

```
    assign q = (state == S0);
```

```
endmodule
```

  

2.4 Parameterized Modules

2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input [width-1:0] d0, d1,
     input              s,
     output [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

Instance with 8-bit bus width (uses default):

```
mux2 myMux(d0, d1, s, out);
```

Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```

2.5 Testbenches

- ★ **HDL that tests another module: *device under test* (dut)**
- ★ **Not synthesizable**
- ★ **Types:**
 - ★ **Simple**
 - ★ **Self-checking**
 - ★ **Self-checking with testvectors**

2.5 Testbench Example

- ★ **Write SystemVerilog code to implement the following function in hardware:**

$$y = \overline{b}\overline{c} + a\overline{b}$$

- ★ **Name the module **sillyfunction****

```
module sillyfunction(input a, b, c,  
                    output y);  
    assign y = ~b & ~c | a & ~b;  
endmodule
```


2.5 Simple Testbench

```
module testbench1();  
    reg a, b, c;  
    wire y;  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
    // apply inputs one at a time  
    initial begin  
        a = 0; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
        a = 1; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
    end  
endmodule
```

2.5 Self-check Testbench

```
module testbench2();
    reg a, b, c;
    wire y;
    sillyfunction dut(a, b, c, y); // instantiate dut
    initial begin //check results one at a time
        a = 0; b = 0; c = 0; #10;
        if (y !== 1) $display("000 failed.");
        c = 1; #10;
        if (y !== 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("010 failed.");
        c = 1; #10;
        if (y !== 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y !== 1) $display("100 failed.");
        c = 1; #10;
        if (y !== 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("110 failed.");
        c = 1; #10;
        if (y !== 0) $display("111 failed.");
    end
endmodule
```

2.5 Testbench with Testvectors

- ★ **Testvector file: inputs and expected outputs**


- ★ **Testbench:**

- ★ **Generate clock for assigning inputs, reading outputs**
- ★ **Read testvectors file into array**
- ★ **Assign inputs, expected outputs**
- ★ **Compare outputs with expected outputs and report errors**

 2.5 Testbench with Testvectors

★ Testbench clock:

- ★ assign inputs (on rising edge)
- ★ compare outputs with expected outputs (on falling edge).



- ★ Testbench clock also used as clock for synchronous sequential circuits

2.5 Testvector File

- ★ **File: example.tv**
- ★ **contains vectors of abc_yexpected**

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```

2.5 (1) Generate Clock

```
module testbench3();  
    reg      clk, reset;  
    reg      a, b, c, yexpected;  
    wire      y;  
    reg [31:0] vectornum, errors; // book keeping variables  
    reg [3:0] testvectors[10000:0]; // array of testvectors  
  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
  
    // generate clock  
    always // no sensitivity list, so it always executes  
        begin  
            clk = 1; #5; clk = 0; #5;  
        end
```

2.5 (2) Read Testvectors into Array

// at start of test, load vectors and pulse reset

```
initial
begin
    $readmemb("example.tv", testvectors);
    vectornum = 0; errors = 0;
    reset = 1; #27; reset = 0;
end
```

// Note: \$readmemb reads testvector files written in
// hexadecimal

2.5 (3) Assign Inputs & Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
    begin
        #1; {a, b, c, yexpected} = testvectors[vectornum];
    end
```


2.5 (4) Compared with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
    if (~reset) begin // skip during reset
        if (y !== yexpected) begin
            $display("Error: inputs = %b", {a, b, c});
            $display("  outputs = %b (%b expected)", y, yexpected);
            errors = errors + 1;
        end
    end
```

```
// Note: to print in hexadecimal, use %h. For example,
//      $display("Error: inputs = %h", {a, b, c});
```

2.5 (4) Compare with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx) begin
    $display("%d tests completed with %d errors",
            vectornum, errors);
    $finish;
end
end
endmodule
```

// === and !== can compare values that are 1, 0, x, or z.