 


数字逻辑设计与微处理器系统

第五讲

Hardware Description Languages

(硬件描述语言)



1.1 Introduction

- ★ **Hardware description language (HDL):**
 - ★ specifies logic function only
 - ★ Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
- ★ **Most commercial designs built using HDLs**
- ★ **Two leading HDLs:**
 - ★ **SystemVerilog/Verilog**
 - ★ developed in 1984 by Gateway Design Automation
 - ★ IEEE standard (1364) in 1995
 - ★ Extended in 2005 (IEEE STD 1800-2009)
 - ★ **VHDL 2008**
 - ★ Developed in 1981 by the Department of Defense
 - ★ IEEE standard (1076) in 1987
 - ★ Updated in 2008 (IEEE STD 1076-2008)

1.1 What & Why HDL?

★ Hardware Description Language(HDL)

- ★ A software programming language used to model the intended operation of a piece of hardware

★ Why HDL?

- ★ Text-based design rather than Schematic design
 - ★ ASIC complexity increase
 - ★ faster time-to-market
- ★ Simulation
- ★ Logic Synthesis
- ★ Words are better than pictures
- ★ PLD, CPLD and FPGA became inexpensive and commonplace

1.1 What is need for HDL ?

★ Model, Represent, And Simulate Digital Hardware

- ★ Hardware Concurrency
- ★ Parallel Activity Flow
- ★ Semantics for Signal Value And Time

★ Special Constructs And Semantics

- ★ Edge Transitions
- ★ Propagation Delays
- ★ Timing Checks

1.1 History of HDL

★ First HDL

- ★ PALASM, 1980s--Logic equation

★ Then more complex (minimization, if-then-else statement)

- ★ CUPL (Compiler Universal for Programmable Logic)
- ★ ABEL (Advanced Boolean Equation Language)

★ VHDL represents another high level language for digital system design.

- ★ VHDL = VHSIC HDL
- ★ VHSIC = Very High Speed Integrated Circuit





1.1 HDLs

- ★ **Software: Assembler → high-level language, like C, C++, Java**
- ★ **Hardware: block diagram & schematic → HDL**
- ★ **Efficient → Large, complex, abstraction**
- ★ **HDL Tool Suits**
 - ★ **Text editor**
 - ★ **Compiler**
 - ★ **Synthesizer**
 - ★ **Simulator**
 - ★ **Template generator**
 - ★ **Schematic viewer**
 - ★ **Translator**
 - ★ **Timing analyzer**
 - ★ **Back annotator**

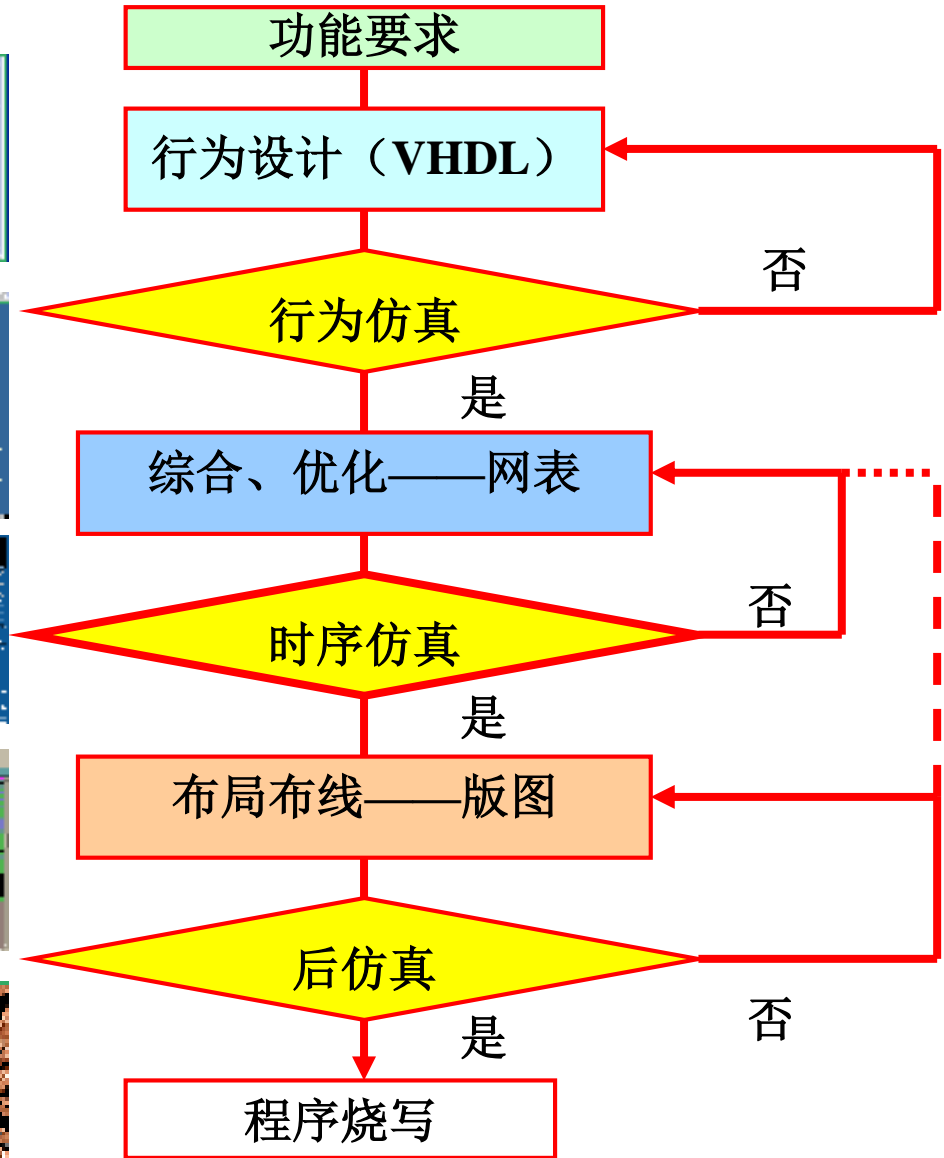   
1.1 Design flow

设计创意
+
仿真验证

```
process begin  
    use is until not  
        CL_OCLK_enable  
        and CL_OCLK=1;  
    if (EN_ALEH=1) then  
        TOGGLEH=not  
        TOGGLEH;  
    end if;  
end process;
```



Levels of Abstraction

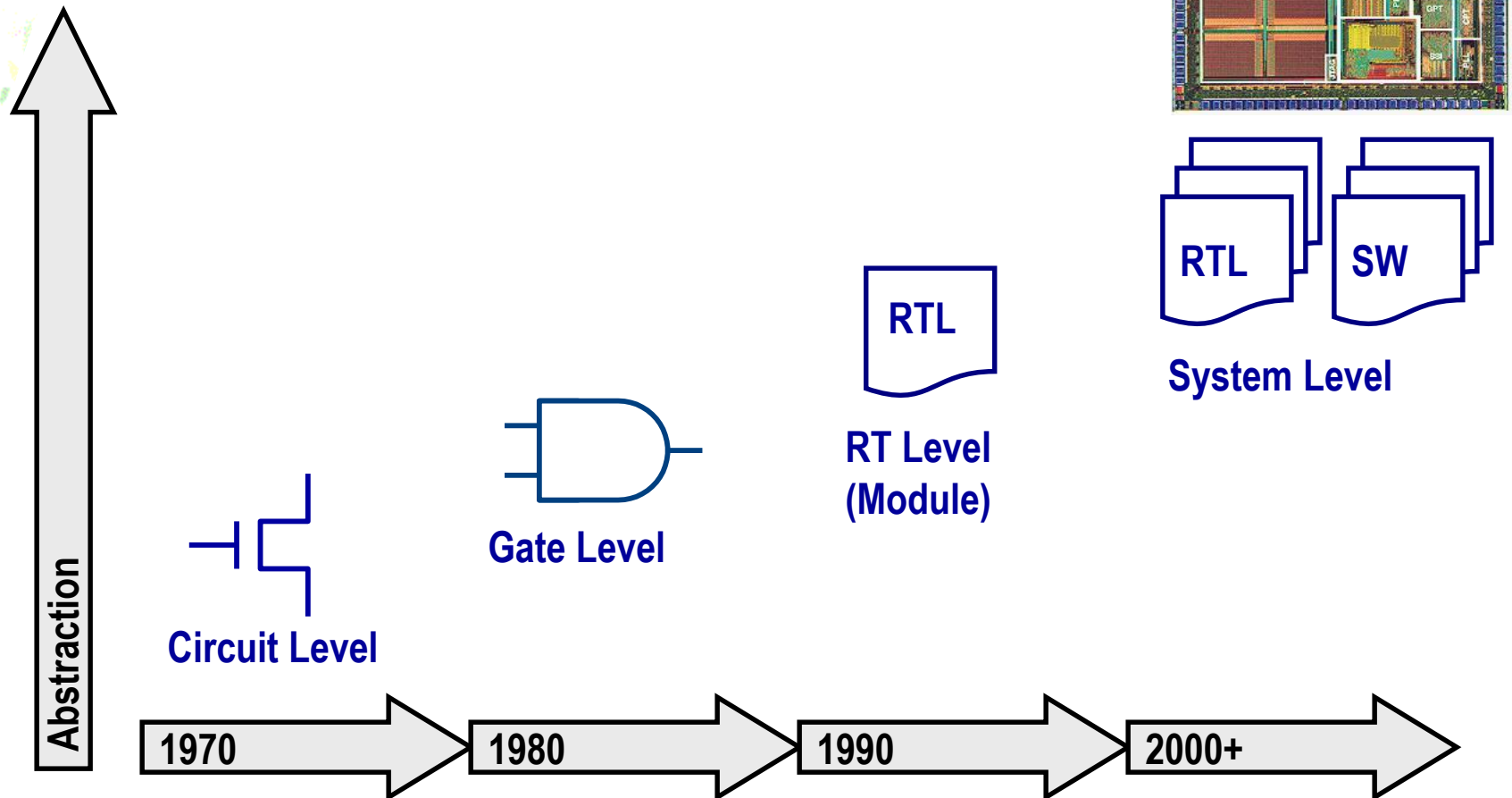

Role of HDLs

★ Design Specification

- ★ unambiguous definition of components, functionality and interfaces

★ Design Simulation

- ★ verify system/subsystem performance and functional correctness prior to design implementation

★ Design Synthesis


- ★ automated generation of a hardware design

HDL Benefits

- ★ **Technology independence**
 - ★ portability
 - ★ Reuse
- ★ **Interoperability between multiple levels of abstractions**
- ★ **Cost reduction**
- ★ **Higher Level of Abstraction (hiding details)**
 - ★ The design task become simpler
 - ★ The design is less error prone
 - ★ Productivity is increased


RTL

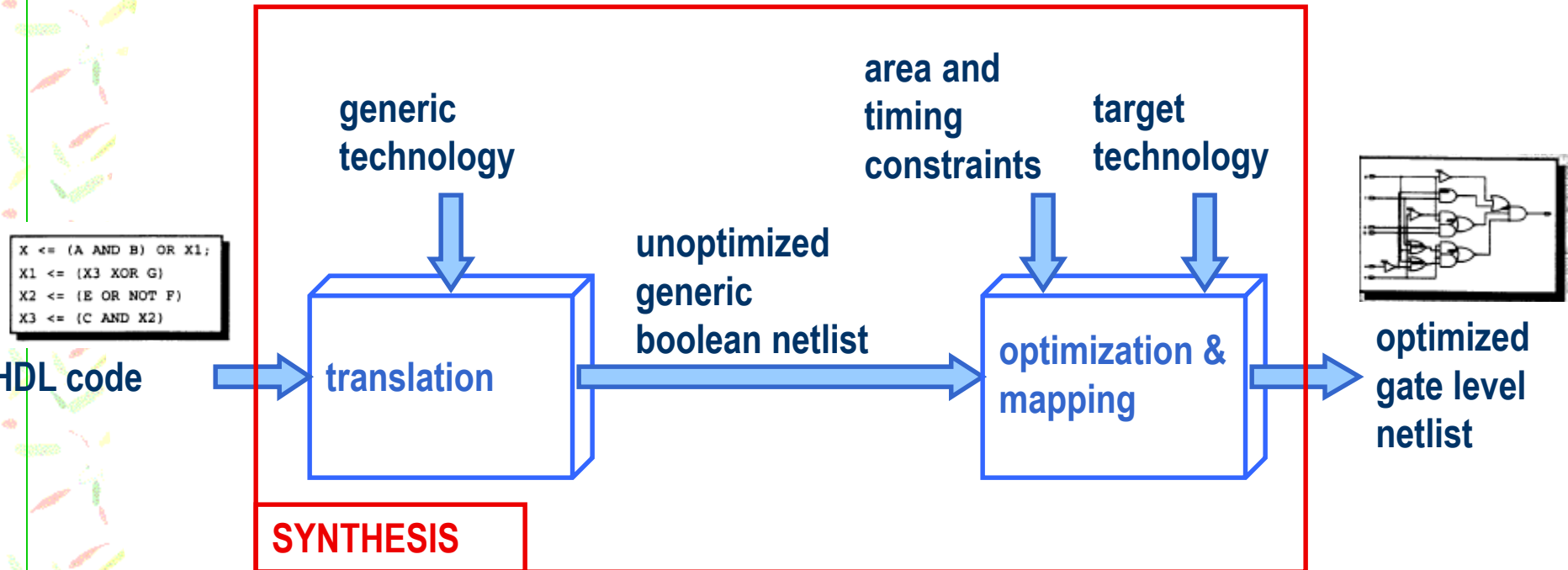- model combinational and sequential logic components
- Only a small subset of the Language statements can be mapped in real “Silicon”.



Structural Level

 - ★ Describe connectivity among components
- ★ The code consists of a bunch of port mappings.






Behavioral Level


- ★ Describe behavior (functionality and performances)
- ★ All language features can be used

Levels of Abstraction

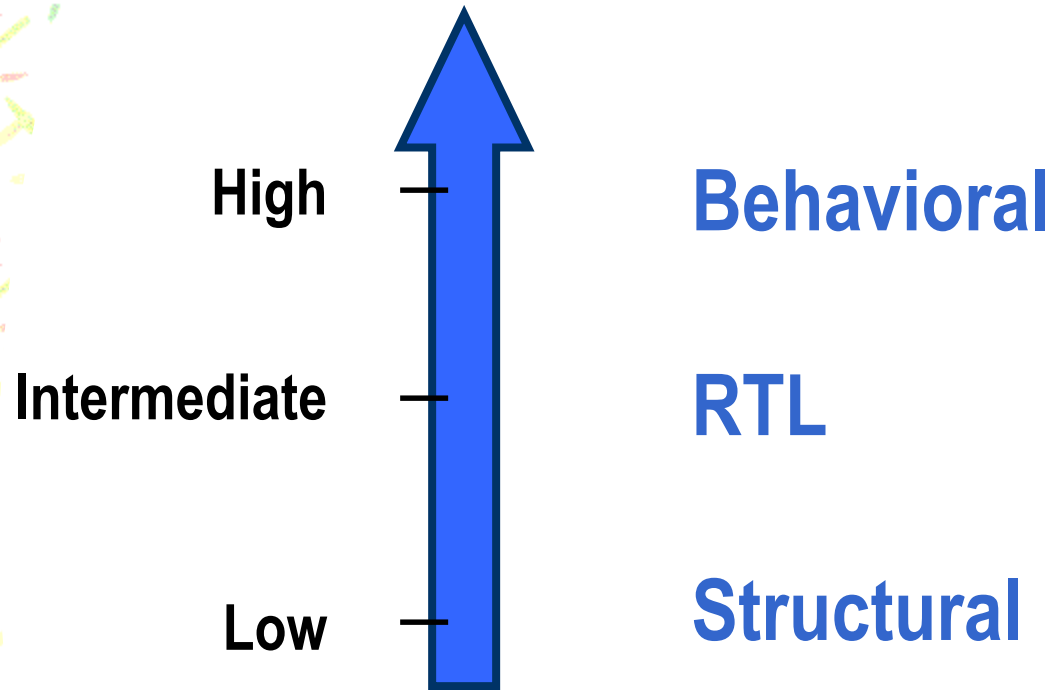

HDL style vs. application

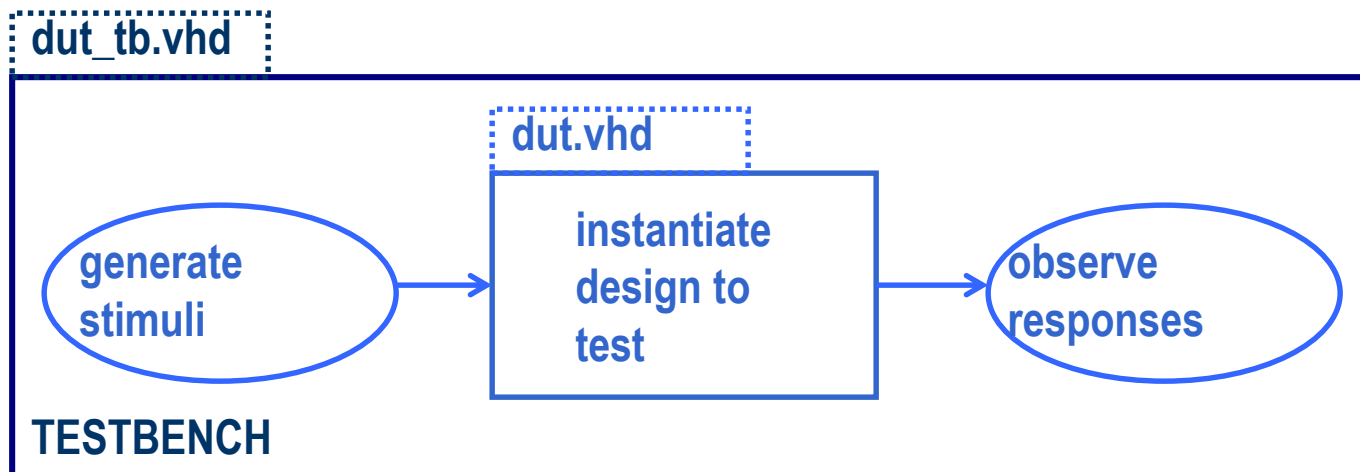- ★ High Level Modeling (Behavioral style)
- ★ Design Entry (Structural & RTL styles)
- ★ Simulation (Behavioral style)
 - ★ validation by mean of a test bench



Modeling Digital Systems

abstraction Levels

- What aspects do we need to consider to describe a digital system ?
 - Interface
 - Function
 - Performance (delay/area/costs/...)

Modeling Digital Systems

- ★ What are the attributes necessary to describe a digital systems ?
 - ★ events, propagation delays, concurrency
 - ★ waveforms and timing
 - ★ signal values
 - ★ shared signals

Modeling Digital Systems

- ★ **Hardware description languages** must provide constructs for describing the attributes of a specific design, and ...
- ★ **Simulators** use such descriptions for “mimicking” the physical system behavior
- ★ **Synthesis compilers** use such descriptions for synthesizing manufacturable hardware that conform to a given specification



HDLs vs. Software Languages

**Concurrent (parallel) Statements
vs.
Sequential Statements**

VHDL Design Organization

- ★ **Entity**

the “symbol” (input/output ports)

- ★ **Architecture**

one of the several possible implementation of the design

- ★ **Configuration**

binding between the symbol and one of the many possible implementation.
Can be used to express hierarchy.

VHDL Design Organization


- ★ **Libraries**

logical units that are mapped to physical directories. The units of a library are called packages.

- ★ **Packages**

repositories for type definitions, procedures, and functions

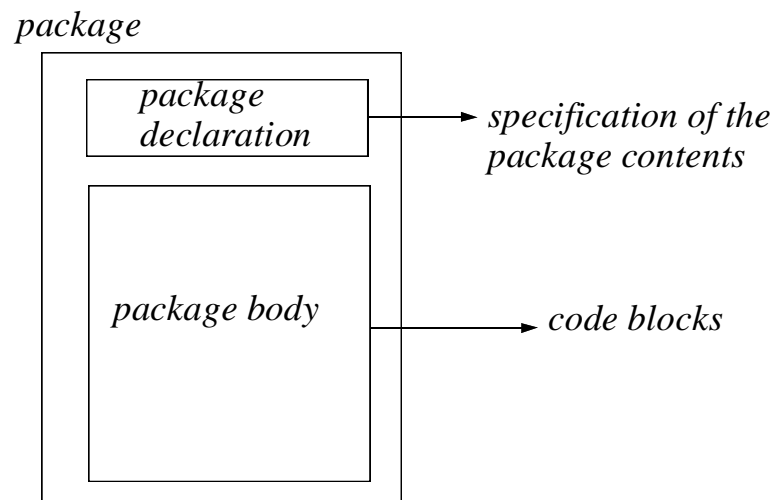- ★ **Libraries and packages can be system defined or user defined**



Bitwise Operation

 


Figure 4.3 inv synthesized circuit


VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity inv is
  port(a:in  STD_LOGIC_VECTOR(3 downto 0);
        y: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of inv is
begin
  y <= not a;
end;
```

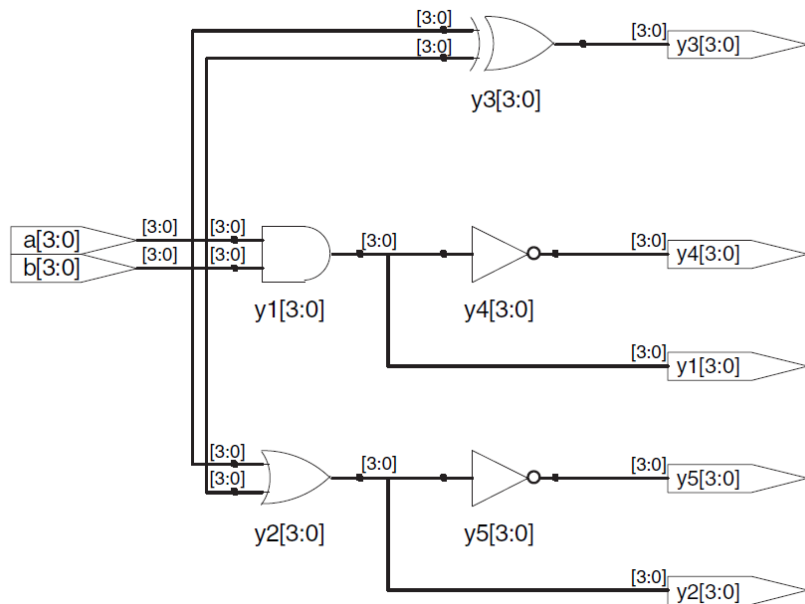VHDL uses `STD_LOGIC_VECTOR` to indicate busses of `STD_LOGIC`. `STD_LOGIC_VECTOR(3 downto 0)` represents a 4-bit bus.



```

library IEEE; use IEEE.STD_LOGIC_1164.all;


entity gates is
port(a, b: in  STD_LOGIC_VECTOR(3 downto 0);
      y1, y2, y3, y4,
      y5:  out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of gates is
begin
  -- five different two-input logic gates
  -- acting on 4-bit busses
  y1 <= a and b;
  y2 <= a or b;
  y3 <= a xor b;
  y4 <= a nand b;
  y5 <= a nor b;
end;


```

VHDL
 
```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity and8 is  
  port(a: in  STD_LOGIC_VECTOR(7 downto 0);  
        y: out STD_LOGIC);  
end;  
  
architecture synth of and8 is  
begin  
  y <= and a;  
  -- and a is much easier to write than  
  -- y <= a(7) and a(6) and a(5) and a(4) and  
  --      a(3) and a(2) and a(1) and a(0);  
end;
```



Conditional Assignment

 

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux2 is
    port(d0, d1: in  STD_LOGIC_VECTOR(3 downto 0);
          s:      in  STD_LOGIC;
          y:      out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of mux2 is
begin
    y <= d1 when s else d0;
end;
```


4:1 Multiplexer

A 4:1 multiplexer can select one of four inputs using multiple `else` clauses in the conditional signal assignment.

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux4 is
    port(d0, d1,
          d2, d3: in  STD_LOGIC_VECTOR(3 downto 0);
          s:      in  STD_LOGIC_VECTOR(1 downto 0);
          y:      out STD_LOGIC_VECTOR(3 downto 0));
end;

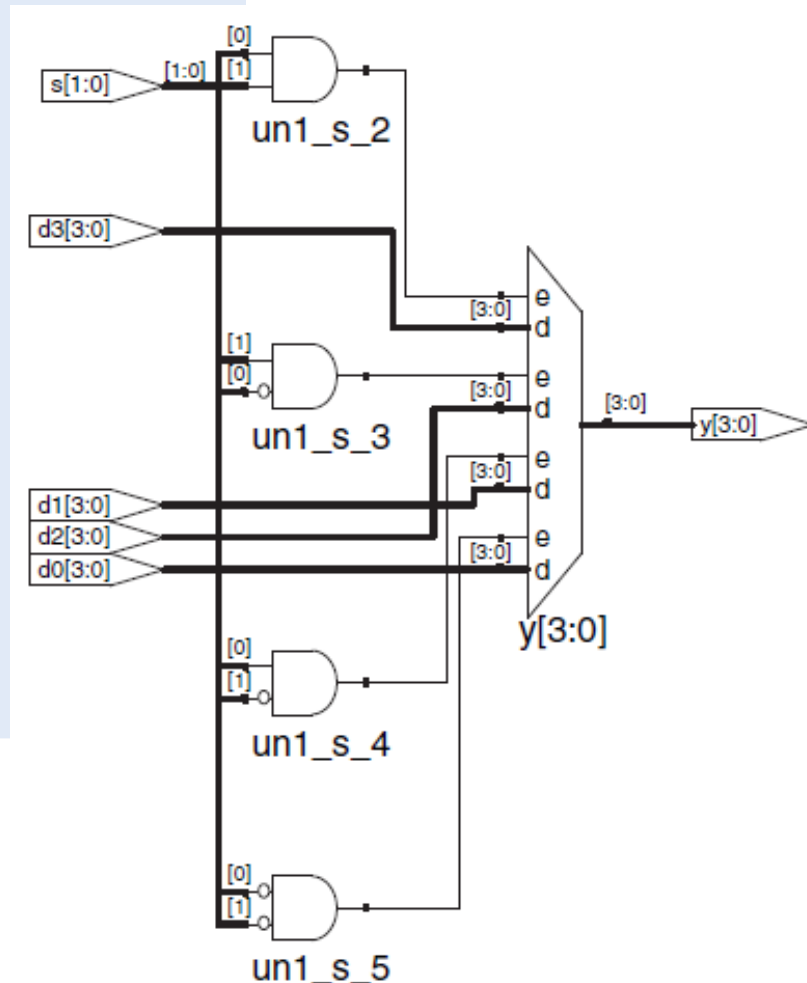architecture synth1 of mux4 is
begin
    y <= d0 when s = "00" else
        d1 when s = "01" else
        d2 when s = "10" else
        d3;
end;
```



Internal signal : Full Adder

$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ C_{out} &= AB + AC_{in} + BC_{in} \end{aligned} \quad (4.1)$$

If we define intermediate signals, P and G ,

$$\begin{aligned} P &= A \oplus B \\ G &= AB \end{aligned} \quad (4.2)$$


we can rewrite the full adder as follows:

$$\begin{aligned} S &= P \oplus C_{in} \\ C_{out} &= G + PC_{in} \end{aligned} \quad (4.3)$$

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
```

```
entity fulladder is  
  port(a, b, cin: in  STD_LOGIC;  
        s, cout:  out STD_LOGIC);  
end;
```
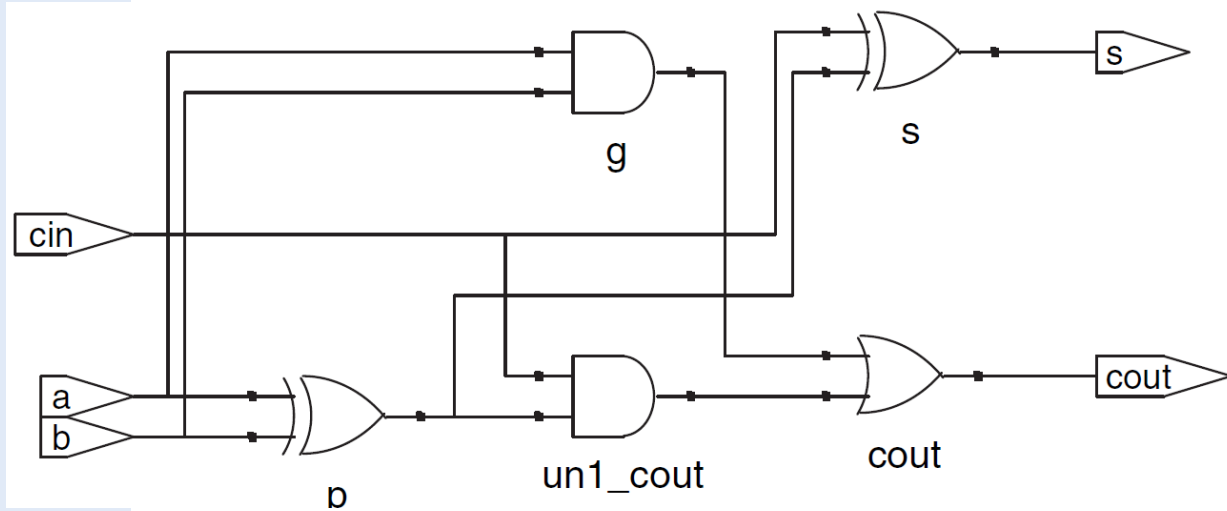
```
architecture synth of fulladder is  
  signal p, g: STD_LOGIC;  
begin  
  p <= a xor b;  
  g <= a and b;  
  
  s <= p xor cin;  
  cout <= g or (p and cin);  
end;
```



Operator

Table 4.2 VHDL operator precedence

	Op	Meaning
Highest	not	NOT
	*, /, mod, rem	MUL, DIV, MOD, REM
	+, -	PLUS, MINUS
	rol, ror, srl, sll	Rotate, Shift logical
	<, <=, >, >=	Relative Comparison
Lowest	=, /=	Equality Comparison
	and, or, nand, nor, xor, xnor	Logical Operations

Multiplication has precedence over addition in VHDL, as you would expect. However, unlike SystemVerilog, all of the logical operations (and, or, etc.) have equal precedence, unlike what one might expect in Boolean algebra. Thus, parentheses are necessary; otherwise `cout <= g or p and cin` would be interpreted from left to right as `cout <= (g or p) and cin`.

Number

Table 4.4 VHDL numbers


Numbers	Bits	Base	Val	Stored
3B"101"	3	2	5	101
B"11"	2	2	3	11
8B"11"	8	2	3	00000011
8B"1010_1011"	8	2	171	10101011
3D"6"	3	10	6	110
6O"42"	6	8	34	100010
8X"AB"	8	16	171	10101011
"101"	3	2	5	101
B"101"	3	2	5	101
X"AB"	8	16	171	10101011

Delay


```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity example is
  port(a, b, c: in  STD_LOGIC;
        y:          out STD_LOGIC);
end;

 architecture synth of example is
  signal ab, bb, cb, n1, n2, n3: STD_LOGIC;
begin
  ab <= not a after 1 ns;
  bb <= not b after 1 ns;
  cb <= not c after 1 ns;
  n1 <= ab and bb and cb after 2 ns;
  n2 <= a and bb and cb after 2 ns;
  n3 <= a and bb and c after 2 ns;
  y  <= n1 or n2 or n3 after 4 ns;
end;
```



Structural Modeling

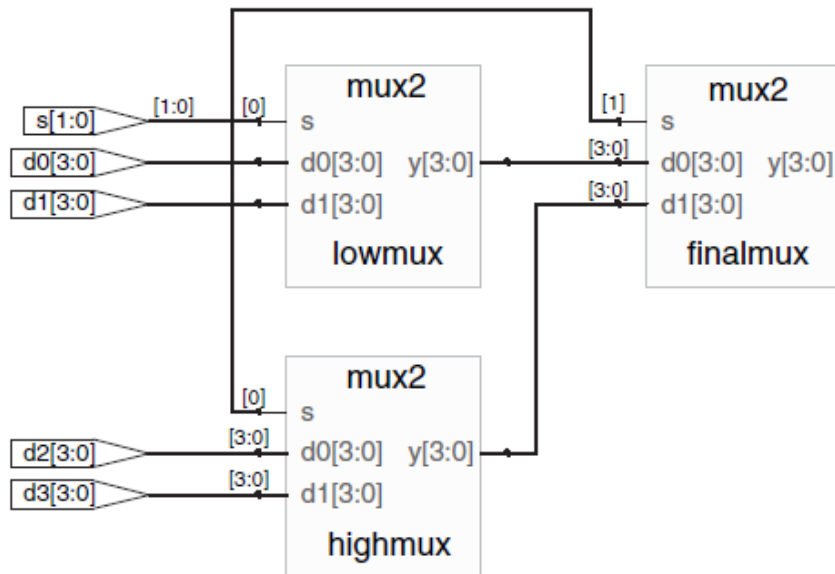

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux4 is
    port(d0, d1,
          d2, d3: in  STD_LOGIC_VECTOR(3 downto 0);
          s:      in  STD_LOGIC_VECTOR(1 downto 0);
          y:      out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture struct of mux4 is
    component mux2
        port(d0,
              d1: in  STD_LOGIC_VECTOR(3 downto 0);
              s:  in  STD_LOGIC;
              y:  out STD_LOGIC_VECTOR(3 downto 0));
    end component;
    signal low, high: STD_LOGIC_VECTOR(3 downto 0);
begin
    lowmux:  mux2 port map(d0, d1, s(0), low);
    highmux: mux2 port map(d2, d3, s(0), high);
    finalmux: mux2 port map(low, high, s(1), y);
end;
    
```

Sequential Logic

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flop is
  port(clk: in  STD_LOGIC;
        d:  in  STD_LOGIC_VECTOR(3 downto 0);
        q:  out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of flop is
begin
  process(clk) begin
    if rising_edge(clk) then
      q <= d;
    end if;
  end process;
end;
```

A VHDL process is written in the form

```
process(sensitivity list) begin
  statement;
end process;
```



`rising_edge(clk)` is synonymous with `clk'event` and `clk = '1'`.

Resettable Register

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flopr is
    port(clk, reset: in  STD_LOGIC;
          d:             in  STD_LOGIC_VECTOR(3 downto 0);
          q:             out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture asynchronous of flopr is
begin
    process(clk, reset) begin
        if reset then
            q <= "0000";
        elsif rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;
```

Resettable Register

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flopr is
  port(clk, reset: in  STD_LOGIC;
        d:           in  STD_LOGIC_VECTOR(3 downto 0);
        q:           out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synchronous of flopr is
begin
  process(clk) begin
    if rising_edge(clk) then
      if reset then q <= "0000";
      else q <= d;
      end if;
    end if;
  end process;
end;
```


Resettable Register

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity flopenr is
    port(clk,
          reset,
          en: in  STD_LOGIC;
          d:  in  STD_LOGIC_VECTOR(3 downto 0);
          q:  out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture asynchronous of flopenr is
    -- asynchronous reset
    begin
        process(clk, reset) begin
            if reset then
                q <= "0000";
            elsif rising_edge(clk) then
                if en then
                    q <= d;
                end if;
            end if;
        end process;
    end;
```

Multiple Register

 

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sync is
    port(clk: in  STD_LOGIC;
          d:   in  STD_LOGIC;
          q:   out STD_LOGIC);
end;

architecture good of sync is
    signal n1: STD_LOGIC;
begin
    process(clk) begin
        if rising_edge(clk) then
            n1 <= d;
            q <= n1;
        end if;
    end process;
end;
```

Process

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity inv is
  port(a: in  STD_LOGIC_VECTOR(3 downto 0);
        y: out STD_LOGIC_VECTOR(3 downto 0));
end;
```

```
architecture proc of inv is
begin
  process(all) begin
    y <= not a;
  end process;
end;
```

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fulladder is
  port(a, b, cin: in  STD_LOGIC;
        s, cout:  out STD_LOGIC);
end;
```

```
architecture synth of fulladder is
begin
  process(all)
    variable p, g: STD_LOGIC;
  begin
    p := a xor b; -- blocking
    g := a and b; -- blocking
    s <= p xor cin;
    cout <= g or (p and cin);
  end process;
end;
```

Process

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity seven_seg_decoder is
    port(data:      in  STD_LOGIC_VECTOR(3 downto 0);
          segments: out STD_LOGIC_VECTOR(6 downto 0));
end;

architecture synth of seven_seg_decoder is
begin
    process(all) begin
        case data is
            --
            --
            when X"0" => segments <= "1111110";
            when X"1" => segments <= "0110000";
            when X"2" => segments <= "1101101";
            when X"3" => segments <= "1111001";
            when X"4" => segments <= "0110011";
            when X"5" => segments <= "1011011";
            when X"6" => segments <= "1011111";
            when X"7" => segments <= "1110000";
            when X"8" => segments <= "1111111";
            when X"9" => segments <= "1110011";
            when others => segments <= "0000000";
        end case;
    end process;
end;
```

Process

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity decoder3_8 is
    port(a: in  STD_LOGIC_VECTOR(2 downto 0);
         y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of decoder3_8 is
begin
    process(all) begin
        case a is
            when "000" => y <= "00000001";
            when "001" => y <= "00000010";
            when "010" => y <= "00000100";
            when "011" => y <= "00001000";
            when "100" => y <= "00010000";
            when "101" => y <= "00100000";
            when "110" => y <= "01000000";
            when "111" => y <= "10000000";
            when others => y <= "XXXXXXXX";
        end case;
    end process;
end;
```


Process

VHDL

1. Use `process(clk)` and nonblocking assignments to model synchronous sequential logic.

```
process(clk) begin
  if rising_edge(clk) then
    n1 <= d; -- nonblocking
    q <= n1; -- nonblocking
  end if;
end process;
```

2. Use concurrent assignments outside process statements to model simple combinational logic.

```
y <= d0 when s = '0' else d1;
```

3. Use `process(all)` to model more complicated combinational logic where the process is helpful. Use blocking assignments for internal variables.

```
process(all)
  variable p, g: STD_LOGIC;
begin
  p := a xor b; -- blocking
  g := a and b; -- blocking
  s <= p xor cin;
  cout <= g or (p and cin);
end process;
```

4. Do not make assignments to the same variable in more than one process or concurrent assignment statement.

Process


```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fulladder is
    port(a, b, cin: in  STD_LOGIC;
          s, cout:  out STD_LOGIC);
end;


architecture nonblocking of fulladder is
    signal p, g: STD_LOGIC;
begin
    process(all) begin
        p <= a xor b; -- nonblocking
        g <= a and b; -- nonblocking
        s <= p xor cin;
        cout <= g or (p and cin);
    end process;
end;
```

Process
 
```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity syncbad is  
  port(clk: in  STD_LOGIC;  
        d:   in  STD_LOGIC;  
        q:   out STD_LOGIC);  
end;  
  
architecture bad of syncbad is  
begin  
  process(clk)  
    variable n1: STD_LOGIC;  
  begin  
    if rising_edge(clk) then  
      n1 := d; -- blocking  
      q <= n1;  
    end if;  
  end process;  
end;
```



State Machine

 

```

library IEEE; use IEEE.STD_LOGIC_1164.all;



entity divideby3FSM is
    port(clk, reset: in  STD_LOGIC;
          y:              out STD_LOGIC);
end;

architecture synth of divideby3FSM is
    type statype is (S0, S1, S2);
    signal state, nextstate: statype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    nextstate <= S1 when state = S0 else
                S2 when state = S1 else
                S0;

    -- output logic
    y <= '1' when state = S0 else '0';
end;
    
```

State Machine

  

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity patternMoore is
  port(clk, reset: in  STD_LOGIC;
        a:           in  STD_LOGIC;
        y:           out STD_LOGIC);
end;

architecture synth of patternMoore is
  type statetype is (S0, S1, S2);
  signal state, nextstate: statetype;
begin
  -- state register
  process(clk, reset) begin
    if reset then          state <= S0;
    elsif rising_edge(clk) then state <= nextstate;
    end if;
  end process;

  -- next state logic
  process(all) begin
    case state is
      when S0 =>
        if a then nextstate <= S0;
        else      nextstate <= S1;
        end if;
      when S1 =>
        if a then nextstate <= S2;
        else      nextstate <= S1;
        end if;
      when S2 =>
        if a then nextstate <= S0;
        else      nextstate <= S1;
        end if;
      when others =>
        nextstate <= S0;
    end case;
  end process;

  --output logic
  y <= '1' when state=S2 else '0';
end;
  
```

Parameterized

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux2 is
  generic(width: integer := 8);
  port(d0,
       d1: in  STD_LOGIC_VECTOR(width-1 downto 0);
       s:  in  STD_LOGIC;
       y:  out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synth of mux2 is
begin
  y <= d1 when s else d0;
end;
```

The generic statement includes a default value (8) of width. The value is an integer.

```
lowmux: mux2 generic map(12)
  port map(d0, d1, s(0), low);
himux:  mux2 generic map(12)
  port map(d2, d3, s(0), hi);
outmux: mux2 generic map(12)
  port map(low, hi, s(1), y);
```

Parameterized

PARAMETERIZED $N:2^N$ DECODER

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;


entity decoder is
  generic(N: integer := 3);
  port(a: in  STD_LOGIC_VECTOR(N-1 downto 0);
        y: out STD_LOGIC_VECTOR(2**N-1 downto 0));
end;

architecture synth of decoder is
begin
  process(all)
  begin
    y <= (OTHERS => '0');
    y(TO_INTEGER(a)) <= '1';
  end process;
end;
```

$2^{**}N$ indicates 2^N .

Parameterized

PARAMETERIZED $N:2^N$ DECODER

 

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity andN is
    generic(width: integer := 8);
    port(a: in  STD_LOGIC_VECTOR(width-1 downto 0);
          y: out STD_LOGIC);
end;

architecture synth of andN is
    signal x: STD_LOGIC_VECTOR(width-1 downto 0);
begin
    x(0) <= a(0);
    gen: for i in 1 to width-1 generate
        x(i) <= a(i) and x(i-1);
    end generate;
    y <= x(width-1);
end;
```


Testbenches

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity testbench1 is -- no inputs or outputs
end;

architecture sim of testbench1 is
  component sillyfunction
    port(a, b, c: in  STD_LOGIC;
         y:          out STD_LOGIC);
  end component;
  signal a, b, c, y: STD_LOGIC;
begin
  -- instantiate device under test
  dut: sillyfunction port map(a, b, c, y);

  -- apply inputs one at a time
  process begin
    a <= '0'; b <= '0'; c <= '0'; wait for 10 ns;
    c <= '1';                               wait for 10 ns;
    b <= '1'; c <= '0';                       wait for 10 ns;
    c <= '1';                               wait for 10 ns;
    a <= '1'; b <= '0'; c <= '0'; wait for 10 ns;
    c <= '1';                               wait for 10 ns;
    b <= '1'; c <= '0';                       wait for 10 ns;
    c <= '1';                               wait for 10 ns;
    wait; -- wait forever
  end process;
end;
```

Consider testing the `sillyfunction` module from [Section 4.1.1](#) that computes $y = \overline{a}\overline{b}\overline{c} + a\overline{b}\overline{c} + a\overline{b}c$. This is a simple module, so we can perform exhaustive testing by applying all eight possible test vectors.

Testbenches

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity testbench2 is -- no inputs or outputs
end;

architecture sim of testbench2 is
    component sillyfunction
        port(a, b, c: in  STD_LOGIC;
             y:          out STD_LOGIC);
    end component;
    signal a, b, c, y: STD_LOGIC;
begin
    -- instantiate device under test
    dut: sillyfunction port map(a, b, c, y);

    -- apply inputs one at a time
    -- checking results
```

```
process begin
    a <= '0'; b <= '0'; c <= '0'; wait for 10 ns;
    assert y = '1' report "000 failed.";
    c <= '1'; wait for 10 ns;
    assert y = '0' report "001 failed.";
    b <= '1'; c <= '0'; wait for 10 ns;
    assert y = '0' report "010 failed.";
    c <= '1'; wait for 10 ns;
    assert y = '0' report "011 failed.";
    a <= '1'; b <= '0'; c <= '0'; wait for 10 ns;
    assert y = '1' report "100 failed.";
    c <= '1'; wait for 10 ns;
    assert y = '1' report "101 failed.";
    b <= '1'; c <= '0'; wait for 10 ns;
    assert y = '0' report "110 failed.";
    c <= '1'; wait for 10 ns;
    assert y = '0' report "111 failed.";
    wait; -- wait forever
end process;
end;
```

Testbenches

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_TEXTIO.ALL; use STD.TEXTIO.all;

entity testbench3 is -- no inputs or outputs
end;

architecture sim of testbench3 is
  component sillyfunction
    port(a, b, c: in  STD_LOGIC;
         y:          out STD_LOGIC);
  end component;
  signal a, b, c, y:  STD_LOGIC;
  signal y_expected: STD_LOGIC;
  signal clk, reset: STD_LOGIC;
begin
  -- instantiate device under test
  dut: sillyfunction port map(a, b, c, y);

  -- generate clock
  process begin
    clk <= '1'; wait for 5 ns;
    clk <= '0'; wait for 5 ns;
  end process;

  -- at start of test, pulse reset
  process begin
    reset <= '1'; wait for 27 ns; reset <= '0';
    wait;
  end process;
```

```
process is
  file tv: text;
  variable L: line;
  variable vector_in: std_logic_vector(2 downto 0);
  variable dummy: character;
  variable vector_out: std_logic;
  variable vectornum: integer := 0;
  variable errors: integer := 0;
begin
  FILE_OPEN(tv, "example.tv", READ_MODE);
  while not endfile(tv) loop

    -- change vectors on rising edge
    wait until rising_edge(clk);

    -- read the next line of testvectors and split into
    readline(tv, L);
    read(L, vector_in);
    read(L, dummy); -- skip over underscore
```

Testbenches

```
read(L, vector_out);
(a, b, c) <= vector_in(2 downto 0) after 1 ns;
y_expected <= vector_out after 1 ns;

-- check results on falling edge
wait until falling_edge(clk);

if y /= y_expected then
    report "Error: y=" & std_logic'image(y);
    errors := errors+1;
end if;

vectornum := vectornum+1;
end loop;

-- summarize results at end of simulation
if (errors=0) then
    report "NO ERRORS -- " &
        integer'image(vectornum) &
        " tests completed successfully."
        severity failure;
else
    report integer'image(vectornum) &
        " tests completed, errors=" &
        integer'image(errors)
        severity failure;
end if;
end process;
end;
```